

ET5302701

Homework Assignment # 3

Date: November 1, 2024

Instructor: M. B. Lin

Due Date: November 22, 2024

Homework is due **at the class beginning**. Please note that **NO late homework** will be accepted. Working together on homework is encouraged, but copying assignments will not be allowed.

1. (A study of inverter circuits)

- (a) Design an inverter with the following circuit parameters: $L_p = L_n = L_{min}$ and $W_p = W_n = W_{min}$. Draw the schematic and the physical layout of the inverter and then perform the LVS check and extract the parameters from the physical layout.
- (b) Cascade three copies of the above inverter.
- (c) Apply an ideal square wave (that is, both rise and fall times are set to 0 ns) with the 50% duty cycle of an appropriate frequency to the input of the first stage and measure the propagation delay of the second stage.
- (d) Repeat above steps with the following circuit parameters: $W_n = W_{min}$ and $W_p = 2W_{min}$.
- (e) Compare both results and give your comments.

2. (A study of path delays)

- (a) Draw the schematic diagram of a three-stage logic circuit with a load capacitor of 0.5 pF. The output of the two-input NOR gate is connected to an inverter and the output of the inverter is in turn connected to one input of a two-input NAND gate. The output of the NAND gate drives the load capacitor. Suppose that the channel lengths and widths of all transistors are set as follows: $L_{(all\ gates)} = L_{min}$, $W_{p(NOR)} = 4W_{min}$, $W_{p(NOT)} = 2W_{min}$, $W_{p(NAND)} = 2W_{min}$, $W_{n(NOR)} = W_{min}$, $W_{n(NOT)} = W_{min}$, $W_{n(NAND)} = 2W_{min}$. The unused inputs of the NAND and NOR gates are connected to V_{DD} and ground, respectively.
- (b) Apply an ideal square wave (that is, both rise and fall times are set to 0 ns) of an appropriate frequency to the input of the first stage, and measure both t_{pLH} and t_{pHL} of the output of the last stage.
- (c) (FO4 rule) Scale up the W of both pMOS and nMOS transistors for the second and last stages by factors of 4 and 16, respectively, and repeat the above step.
- (d) (Path-delay optimization) Use the method of path-delay optimization, scale up the W of both pMOS and nMOS transistors for each stage, and repeat the above step. Assume that $C_{in} = C_g(W_n + W_p)$.
- (e) Compare the results from (b) to (d) and give your comments.